
REQUIREMENTS NOT MET

N/A

VIDEO FILE LINK

https://drive.google.com/file/d/15XCk-p2LTxNXuliOADmf0P1iI8_1zABs/view?usp=sharing

PROBLEMS ENCOUNTERED

There were no problems encountered.

FUTURE WORK/APPLICATIONS

This lab primarily focused on the functions and uses of the MUX and Decoder (Hex to Seven-Segment Display), these components have several applications in constructing more complex circuits such as in future labs, with the counter and flip flops.

PRE-LAB QUESTIONS OR EXERCISES

PART 1: INTRODUCTION TO MULTIPLEXERS

Table 1: Truth Table for Part 1

S0	D1	D0	Y
0	*	0	0
0	*	1	1
1	0	*	0
1	1	*	1

SOP: $Y = \neg S_0 \cdot D_0 + S_0 \cdot D_1$

POS: $Y = (S_0 + D_0) \cdot (\neg S_0 + D_1)$

Table 2: Voltage Table for Part 1

S0 (H)	D1 (H)	D0 (L)	Y (L)
L	*	H	H
L	*	L	L
H	L	*	H
H	H	*	L

 


Figure 1: 2-input MUX Block Diagram

Lab 2 Part 1

Name: Emilee Zhou

Class #: 11195

PI's Name: Keith Khadar

Description: 2-input MUX

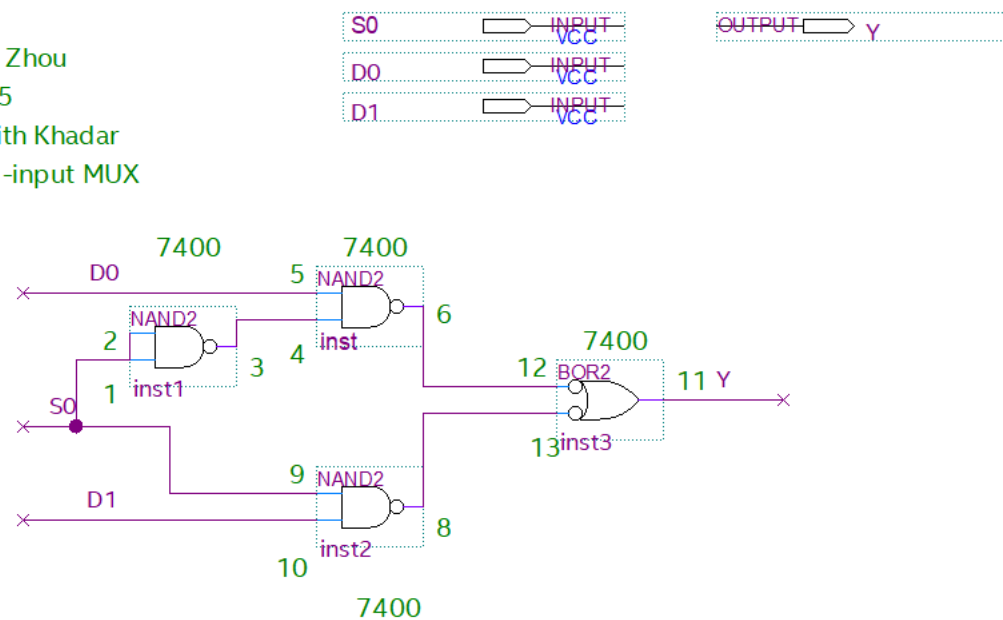


Figure 2: 2-input MUX BDF for Part 1

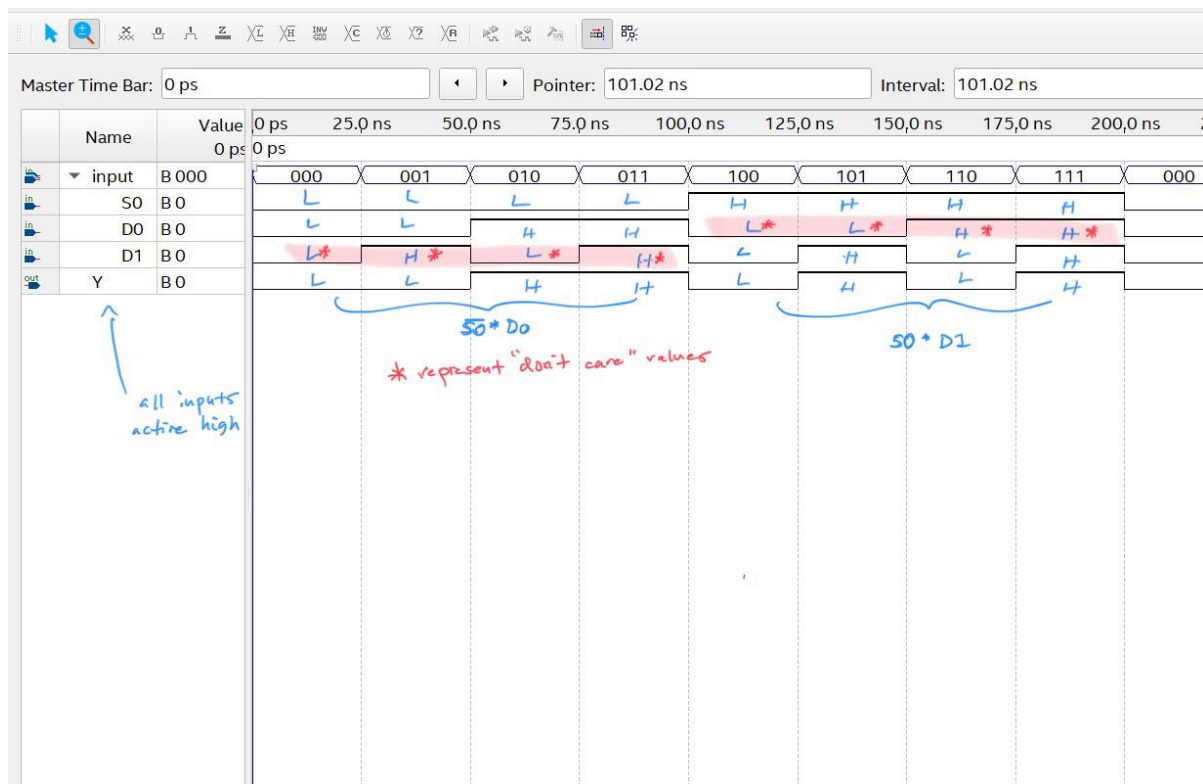


Figure 3: Function Simulation for Part 1

 


Figure 4: Switch and LED Legends for Part 1

PART 2: FOUR-INPUT MULTIPLEXER DESIGN

Table 3: Truth Table for Part 2

S1	S0	D3	D2	D1	D0	Y
0	0	*	*	*	0	0
0	0	*	*	*	1	1
0	1	*	*	0	*	0
0	1	*	*	1	*	1
1	0	*	0	*	*	0
1	0	*	1	*	*	1
1	1	0	*	*	*	0
1	1	1	*	*	*	1

POS: $Y = (/S1 + /S0 + D0) * (/S1 + S0 + D1) * (S1 + /S0 + D2) * (S1 + S0 + D3)$

SOP: $Y = /S1 * /S0 * D0 + /S1 * S0 * D1 + S1 * /S0 * D2 + S1 * S0 * D3$

Table 4: Voltage Table for Part 2

S1(H)	S0(H)	D3(H)	D2(L)	D1(H)	D0(L)	Y(H)
L	L	*	*	*	H	L
L	L	*	*	*	L	H
L	H	*	*	L	*	L
L	H	*	*	H	*	H
H	L	*	H	*	*	L
H	L	*	L	*	*	H
H	H	L	*	*	*	L
H	H	H	*	*	*	H

 


Figure 5: 4-input MUX Block Diagram for Part 2

$$Y = \bar{S}_1 \bar{S}_0 D_0 + \bar{S}_1 S_0 D_1 + S_1 \bar{S}_0 D_2 + S_1 S_0 D_3$$

 


Figure 6: 4-input MUX Diagram for Part 2

Lab 2 Part 2
Name: Emilee Zhou
Class #: 11195
PI's Name: Keith Khadar
Description: 4-input MUX

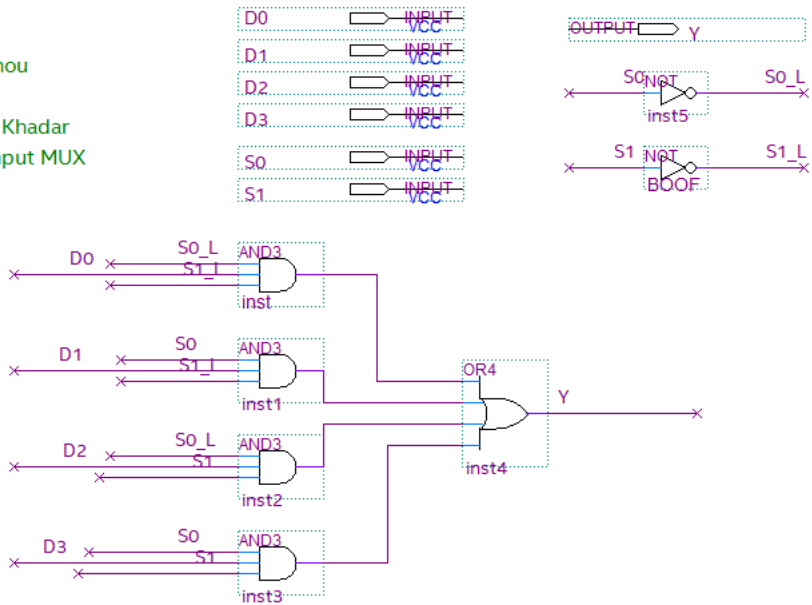


Figure 7: 4-input MUX BDF for Part 2

Lab 2 Part 2
Name: Emilee Zhou
Class #: 11195
PI's Name: Keith Khadar
Description: 4-input MUX

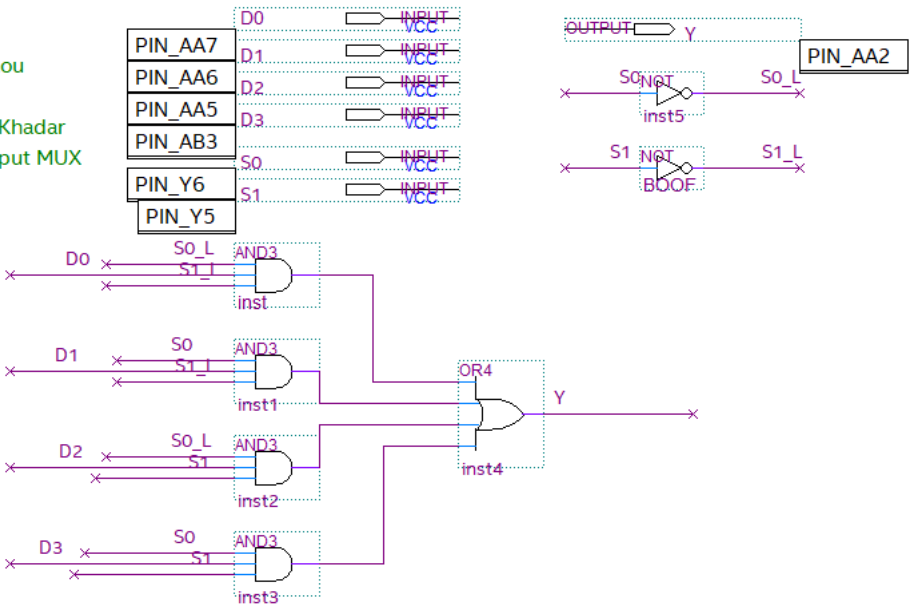


Figure 8: BDF with programmed pins for Part 2








 
Named: * Edit:										
Node Name	Direction	Location	I/O Bank	VREF Group	Fitter Location	I/O Standard	Reserved	Current Strength	Slew Rate	Diff
 D0	Input	PIN_AA7	3	B3_NO	PIN_AA7	2.5 V		12mA (default)		
 D1	Input	PIN_AA6	3	B3_NO	PIN_AA6	2.5 V		12mA (default)		
 D2	Input	PIN_AA5	3	B3_NO	PIN_AA5	2.5 V		12mA (default)		
 D3	Input	PIN_AB3	3	B3_NO	PIN_AB3	2.5 V		12mA (default)		
 S0	Input	PIN_Y6	3	B3_NO	PIN_Y6	2.5 V		12mA (default)		
 S1	Input	PIN_Y5	3	B3_NO	PIN_Y5	2.5 V		12mA (default)		
 Y	Output	PIN_AA2	3	B3_NO	PIN_AA2	2.5 V		12mA (default)	2 (default)	
<<new node>>										

Figure 9: Pin Assignments for Part 2

Table 5: 4-input MUX LED and Switch Legends for Part 2



PART 3: DECODER DESIGN

Table 6: Truth Table for Part 3

T	X3	X2	X1	X0	A	B	C	D	E	F	G
0	0	0	0	0	1	1	1	1	1	1	0
0	0	0	0	1	0	1	1	0	0	0	0
0	0	0	1	0	1	1	0	1	1	0	1
0	0	0	1	1	1	1	1	1	0	0	1
0	0	1	0	0	0	1	1	0	0	1	1
0	0	1	0	1	1	0	1	1	0	1	1
0	0	1	1	0	1	0	1	1	1	1	1
0	0	1	1	1	1	1	1	1	0	0	0
0	1	0	0	0	1	1	1	1	1	1	1
0	1	0	0	1	1	1	1	1	0	1	1
0	1	0	1	0	1	1	1	0	1	1	1
0	1	0	1	1	0	0	1	1	1	1	1
0	1	1	0	0	1	0	0	1	1	1	0
0	1	1	0	1	0	1	1	1	1	0	1
0	1	1	1	0	1	0	0	1	1	1	1
0	1	1	1	1	1	0	0	0	1	1	1
1	*	*	*	*	1	1	1	1	1	1	1

(A) SOP: $\bar{x}_3\bar{x}_2\bar{x}_1\bar{x}_0\bar{T} + \bar{x}_3\bar{x}_2x_1\bar{x}_0\bar{T} + \bar{x}_3\bar{x}_2x_1x_0\bar{T} + \bar{x}_3x_2\bar{x}_1\bar{x}_0\bar{T} + \bar{x}_3x_2x_1\bar{x}_0\bar{T} + \bar{x}_3x_2x_1x_0\bar{T} + x_3\bar{x}_2\bar{x}_1\bar{x}_0\bar{T} + x_3\bar{x}_2\bar{x}_1x_0\bar{T} + x_3\bar{x}_2x_1\bar{x}_0\bar{T} + x_3\bar{x}_2x_1x_0\bar{T} + x_3x_2\bar{x}_1\bar{x}_0\bar{T} + x_3x_2\bar{x}_1x_0\bar{T} + x_3x_2x_1\bar{x}_0\bar{T} + x_3x_2x_1x_0\bar{T} + T$

POS: $(\bar{x}_3 + \bar{x}_2 + \bar{x}_1 + x_0 + \bar{T})(\bar{x}_3 + x_2 + \bar{x}_1 + \bar{x}_0 + \bar{T})(\bar{x}_3 + \bar{x}_2 + x_1 + x_0 + \bar{T})(\bar{x}_3 + x_2 + \bar{x}_1 + x_0 + \bar{T})$

Figure 10: SOP and POS equations for Output A for Part 3

(B) SOP: $\bar{x}_3\bar{x}_2\bar{x}_1\bar{x}_0\bar{T} + \bar{x}_3\bar{x}_2\bar{x}_1x_0\bar{T} + \bar{x}_3\bar{x}_2x_1\bar{x}_0\bar{T} + \bar{x}_3\bar{x}_2x_1x_0\bar{T} + \bar{x}_3x_2\bar{x}_1\bar{x}_0\bar{T} + \bar{x}_3x_2\bar{x}_1x_0\bar{T} + x_3\bar{x}_2\bar{x}_1\bar{x}_0\bar{T} + x_3\bar{x}_2\bar{x}_1x_0\bar{T} + x_3\bar{x}_2x_1\bar{x}_0\bar{T} + x_3\bar{x}_2x_1x_0\bar{T} + x_3x_2\bar{x}_1\bar{x}_0\bar{T} + x_3x_2\bar{x}_1x_0\bar{T} + x_3x_2x_1\bar{x}_0\bar{T} + x_3x_2x_1x_0\bar{T} + T$

POS: $(\bar{x}_3 + x_2 + \bar{x}_1 + x_0 + \bar{T})(\bar{x}_3 + x_2 + \bar{x}_1 + \bar{x}_0 + \bar{T})(\bar{x}_3 + \bar{x}_2 + x_1 + x_0 + \bar{T})(\bar{x}_3 + x_2 + \bar{x}_1 + \bar{x}_0 + \bar{T})(\bar{x}_3 + x_2 + x_1 + \bar{x}_0 + \bar{T})(\bar{x}_3 + x_2 + x_1 + x_0 + \bar{T})$

Figure 11: SOP and POS equations for Output B for Part 3

(C) SOP: $\bar{x}_3\bar{x}_2\bar{x}_1\bar{x}_0\bar{T} + \bar{x}_3\bar{x}_2\bar{x}_1x_0\bar{T} + \bar{x}_3\bar{x}_2x_1\bar{x}_0\bar{T} + \bar{x}_3\bar{x}_2x_1x_0\bar{T} + \bar{x}_3x_2\bar{x}_1\bar{x}_0\bar{T} + \bar{x}_3x_2\bar{x}_1x_0\bar{T} + x_3\bar{x}_2\bar{x}_1\bar{x}_0\bar{T} + x_3\bar{x}_2\bar{x}_1x_0\bar{T} + x_3\bar{x}_2x_1\bar{x}_0\bar{T} + x_3\bar{x}_2x_1x_0\bar{T} + x_3x_2\bar{x}_1\bar{x}_0\bar{T} + x_3x_2\bar{x}_1x_0\bar{T} + x_3x_2x_1\bar{x}_0\bar{T} + x_3x_2x_1x_0\bar{T} + T$

Figure 12: SOP equations for Output A for Part 3

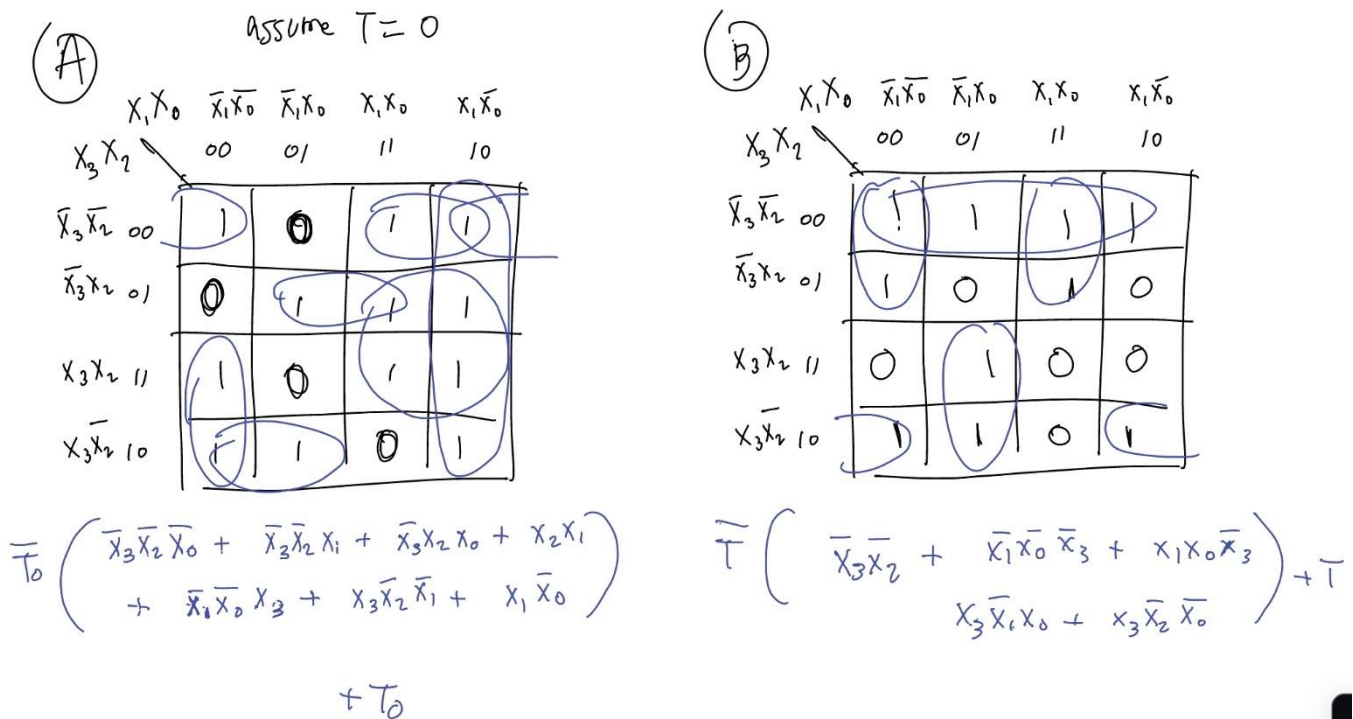


Figure 13: K-Maps for Part 3

Table 7: Voltage Table for Part 3

T (L)	X3 (H)	X2 (H)	X1 (H)	X0 (H)	A (L)	B (L)	C (L)
H	L	L	L	L	L	L	L

H	L	L	L	H	H	L	L
H	L	L	H	L	L	L	H
H	L	L	H	H	L	L	L
H	L	H	L	L	H	L	L
H	L	H	L	H	L	H	L
H	L	H	H	L	L	L	L
H	L	H	H	H	L	L	L
H	H	L	L	L	L	L	L
H	H	L	L	H	L	L	L
H	H	L	H	H	H	H	L
H	H	H	L	L	L	H	H
H	H	H	L	H	H	L	L
H	H	H	H	H	L	H	H
H	H	H	H	H	H	H	H
L	*	*	*	*	L	L	L

 


Figure 14: Block Diagram of Hex to 7-seg Decoder for Part 3

Lab 2 Part 3
Name: Emilee Zhou
Class #: 11195
PI's Name: Keith Khadar
Description: Hex to 7-Segment Display Decoder

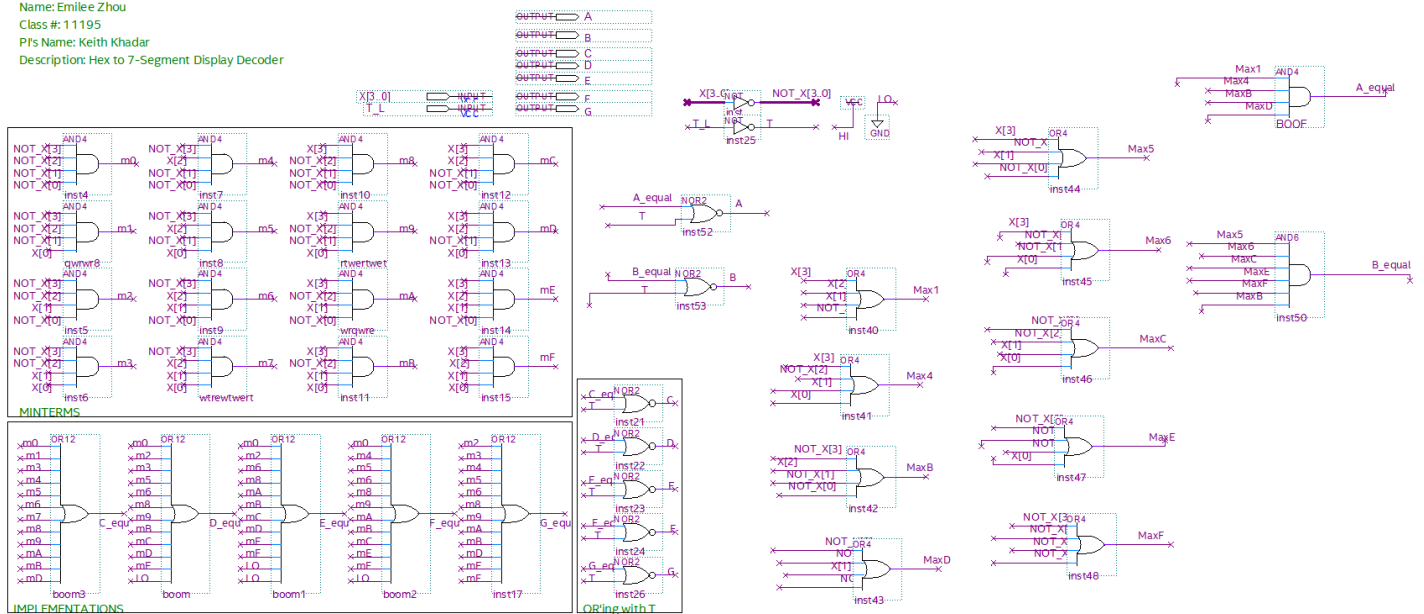


Figure 15: BDF of Hex to 7-Segment Display Decoder for Part 3

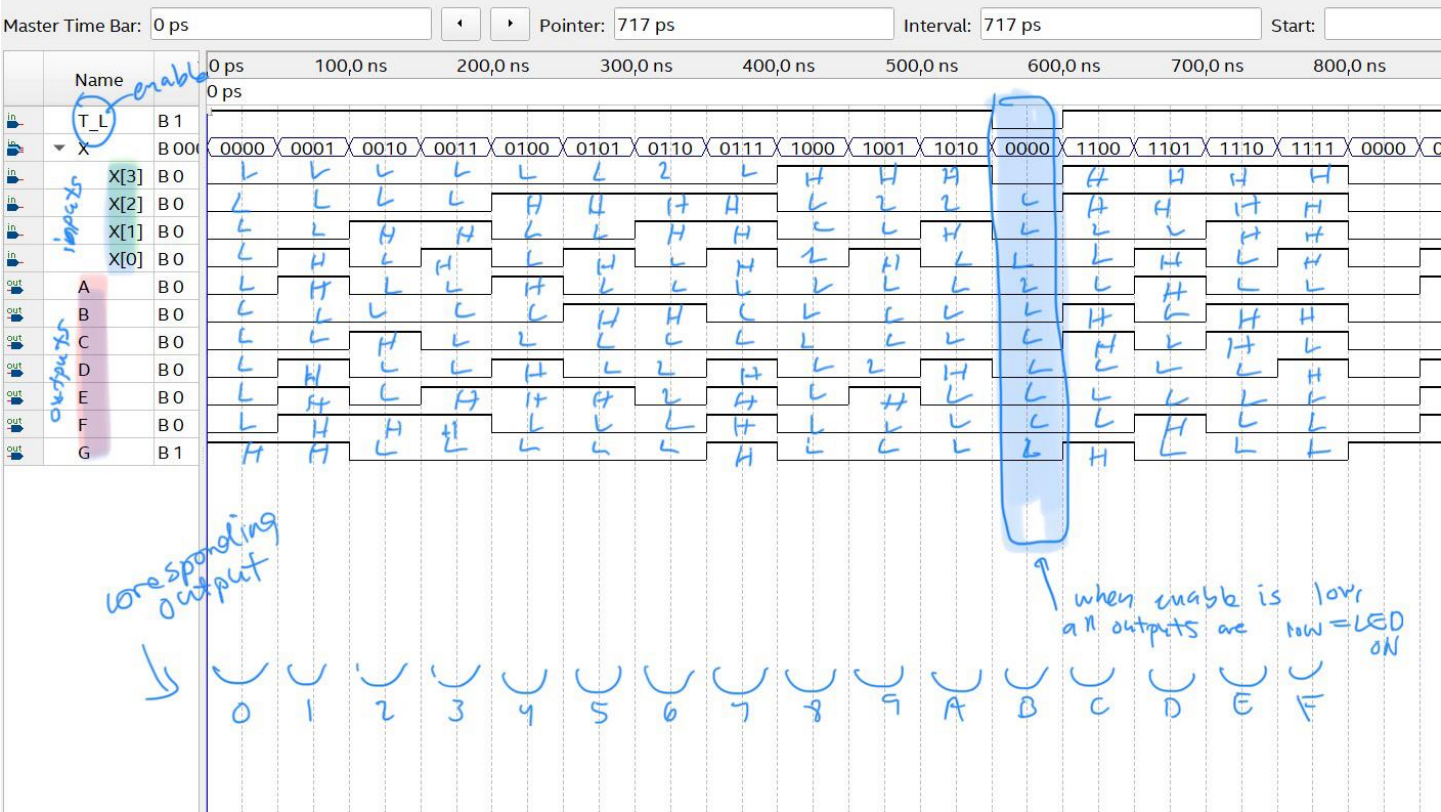


Figure 16: Functional Simulation for Part 3

Node Name	Direction	Location	I/O Bank	VREF Group	Fitter Location	I/O Standard	Reserved	Current Strength	Slew Rate	Differential Pair	Strict Preservati
A	Output	PIN_C14	7	B7_NO	PIN_E8	2.5 V (default)		12mA (default)	2 (default)		
B	Output	PIN_E15	7	B7_NO	PIN_D5	2.5 V (default)		12mA (default)	2 (default)		
C	Output	PIN_C15	7	B7_NO	PIN_B5	2.5 V (default)		12mA (default)	2 (default)		
D	Output	PIN_C16	7	B7_NO	PIN_B2	2.5 V (default)		12mA (default)	2 (default)		
E	Output	PIN_E16	7	B7_NO	PIN_D6	2.5 V (default)		12mA (default)	2 (default)		
F	Output	PIN_D17	7	B7_NO	PIN_C5	2.5 V (default)		12mA (default)	2 (default)		
G	Output	PIN_C17	7	B7_NO	PIN_C4	2.5 V (default)		12mA (default)	2 (default)		
S0	Input	PIN_Y6	3	B3_NO	PIN_A3	2.5 V (default)		12mA (default)			
S1	Input	PIN_Y5	3	B3_NO	PIN_A2	2.5 V (default)		12mA (default)			
T_L	Input	PIN_AB2	3	B3_NO	PIN_E9	2.5 V (default)		12mA (default)			
X[3]	Input	PIN_AB3	3	B3_NO	PIN_D7	2.5 V (default)		12mA (default)			
X[2]	Input	PIN_AA5	3	B3_NO	PIN_B4	2.5 V (default)		12mA (default)			
X[1]	Input	PIN_AA6	3	B3_NO	PIN_B3	2.5 V (default)		12mA (default)			
X[0]	Input	PIN_AA7	3	B3_NO	PIN_C6	2.5 V (default)		12mA (default)			
Y	Output	PIN_AA2	3	B3_NO	PIN_F7	2.5 V (default)		12mA (default)	2 (default)		
<<new node>>											

Figure 17: Pin Assignments for Part 3

 


Figure 18: Switch and LED Legend for Part 3

Lab 2 Part 4

Name: Emilee Zhou

Class #: 11195

PI's Name: Keith Khadar

Description: 2-input MUX

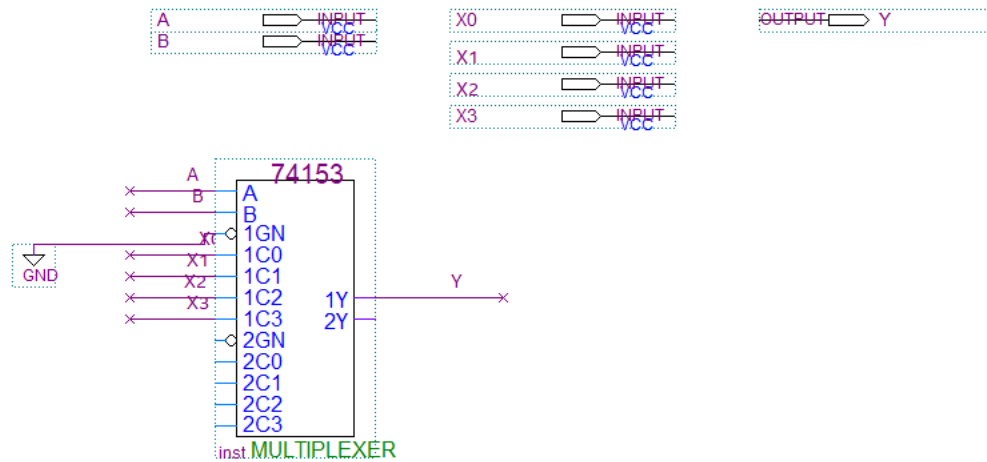


Figure 19: BDF of Double 4-input MUX


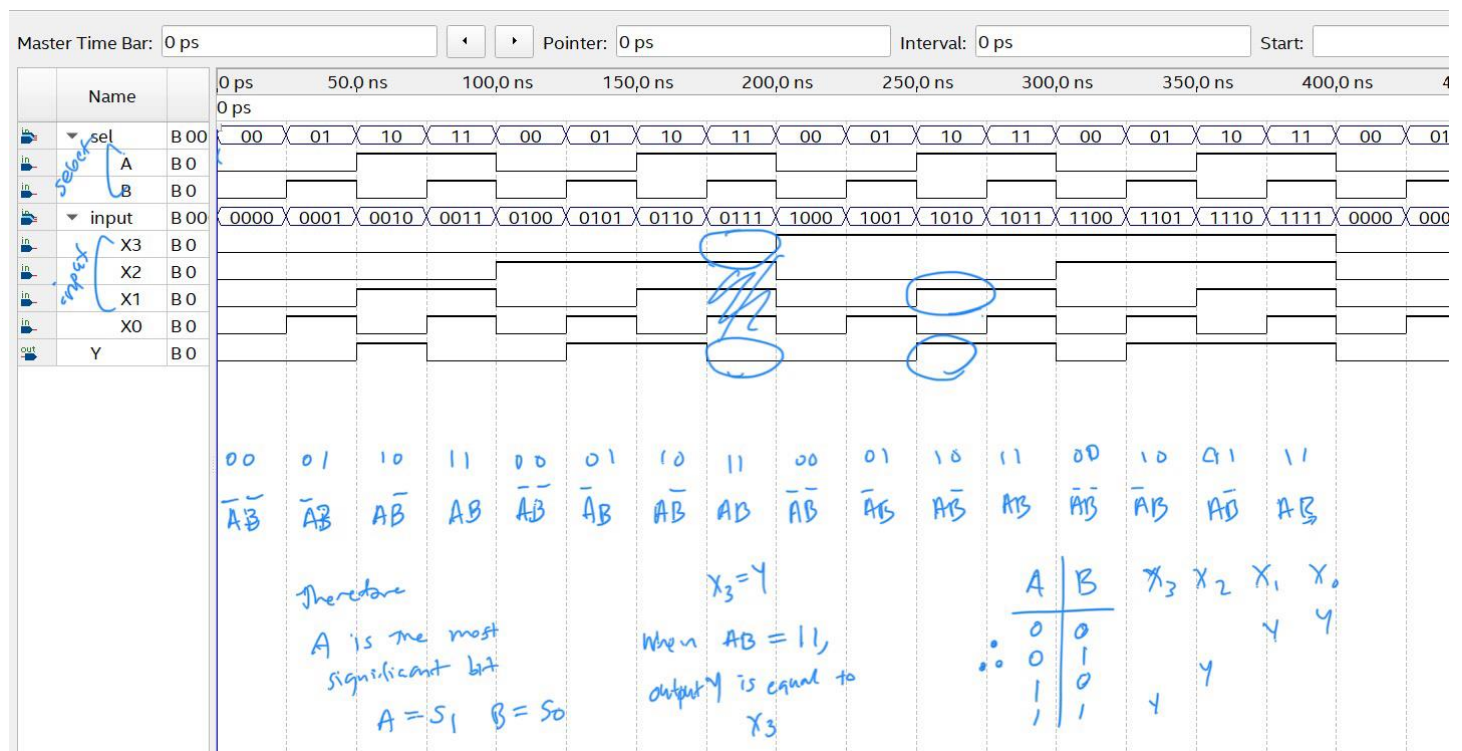


Figure 20: Functional Simulation for Part 4

Table 8: Truth Table for Part 4

V	W	X	Z	/V	/X	/X*Z	(W+/X*Z)	/V*(W+/X*Z)	/V*/W*/X	F
0	0	0	0	1	1	0	0	0	1	1
0	0	0	1	1	1	1	1	1	1	1
0	0	1	0	1	0	0	0	0	0	0
0	0	1	1	1	0	0	0	0	0	0
0	1	0	0	1	1	0	1	1	0	1
0	1	0	1	1	1	1	1	1	0	1
0	1	1	0	1	0	0	1	1	0	1
0	1	1	1	1	0	0	1	1	0	1
1	0	0	0	0	1	0	0	0	0	0
1	0	0	1	0	1	1	1	0	0	0
1	0	1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0
1	1	0	0	0	1	0	1	0	0	0
1	1	0	1	0	1	1	1	0	0	0
1	1	1	0	0	0	0	1	0	0	0
1	1	1	1	0	0	0	1	0	0	0

 

$$MSOP = \overline{X}\overline{V} + \overline{V}W$$

$$\overline{V}(\overline{X} + W)$$

Figure 21: MSOP and K-Map for Part 4

Lab 2 Part 4
Name: Emilee Zhou
Class #: 11195
PI's Name: Keith Khadar
Description: 2-input MUX for eq. F

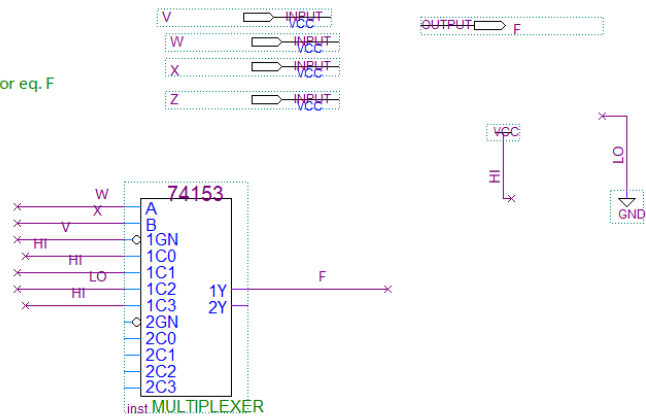


Figure 22: BDF of F for Part 4

Table 9: Voltage Table for Part 4

V(L)	W(H)	X(H)	Z(H)	F(H)
L	*	*	*	L
H	L	L	*	H
H	L	H	*	L
H	H	L	*	H
H	H	H	*	H

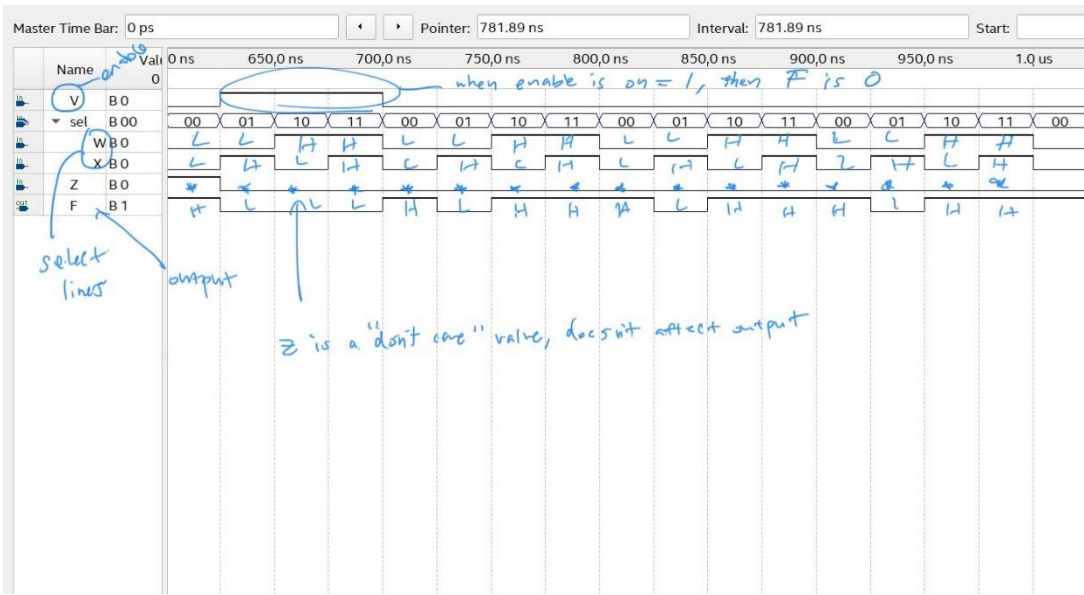


Figure 23: Functional Simulation for Part 4