

---

REQUIREMENTS NOT MET

---

N/A

---

PROBLEMS ENCOUNTERED


---

N/A

HOMWORK EXERCISES

 1. Use a Quartus Simulation to Show that an S-R latch can be made using two NAND gates.

hw7, Part A  
Name: Natalie Poche  
Class #: 111938  
PI Name: Jaiden Magnan  
Description: Make S-R latch with two NAND gates



a.

 


Figure 1: Homework 7 - Part 1: BDF of S-R latch with Two NAND gates

b.


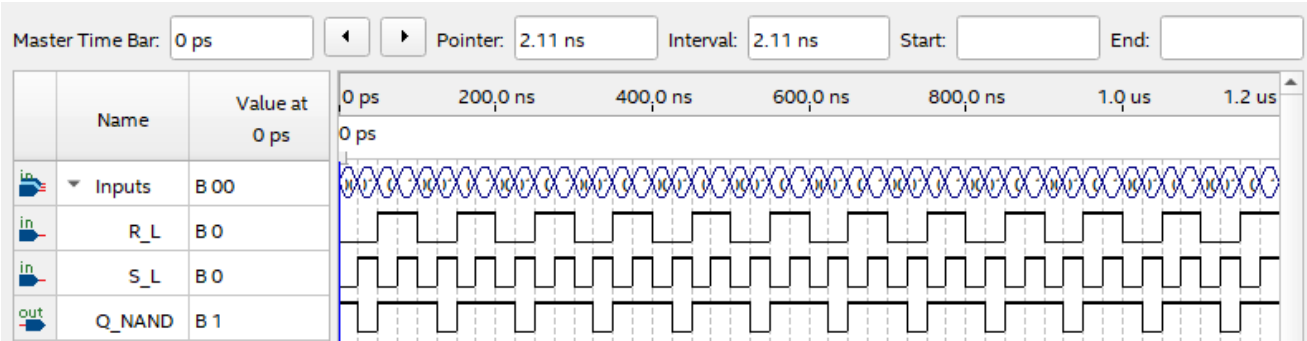
 


Figure 2: Homework 7 - Part 1: Functional Simulation of S-R latch with two NAND gates

 
2. Use a Quartus Simulation to Show that an S-R latch can be made using two NOR gates.

hw7, Part B  
Name: Natalie Poche  
Class #: 11198  
PI Name: Jaiden Magnan  
Description: S-R latch using 2 NOR gates



a.

Figure 3: Homework 7 - Part 2: BDF of S-R latch with Two NOR gates

 


b.

Figure 4: Homework 7 - Part 2: Functional Simulation of S-R latch with Two NOR gates

3. Derive the characteristic equations and excitation tables for each type of flip-flop.

**FIGURE 12-9**  
Typical Timing  
Diagram for  
Shift Register of  
Figure 12-8

© Cengage Learning 2014

 

D Flip Flop	
D	$Q^+$
0	0
1	1

$$Q^+ = D$$

D-FF Excitation Table		
Q	$Q^+$	D
0	0	0
0	1	1
1	0	0
1	1	1

T Flip Flop	
T	$Q^+$
0	Q
1	$/Q$

$$Q^+ = T*Q + /T*/Q$$

T-FF Excitation Table		
Q	$Q^+$	T
0	0	0
0	1	1
1	0	1
1	1	0

SR Flip Flop		
R	T	$Q^+$
0	0	Q
0	1	0
1	0	1

$$Q^+ = S + /R*Q$$

SR-FF Excitation Table			
Q	$Q^+$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

JK Flip Flop		
J	K	$Q^+$
0	0	Q
0	1	0
1	0	1
1	1	$/Q$


$$Q^+ = J*Q + /K*Q$$

JK-FF Excitation Table			
Q	$Q^+$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

4. 7<sup>th</sup> edition Roth Textbook Problem 11.26

 **11.26** The ClrN and PreN inputs introduced in Section 11.8 are called asynchronous because they operate independently of the clock (i.e., they are not synchronized with the clock). We can also make flip-flops with synchronous clears or preset inputs.

A D-flip-flop with an active-low synchronous ClrN input may be constructed from a regular D flip-flop as follows.



Fill in the timing diagram. For  $Q_1$ , assume a synchronous ClrN as above, and for  $Q_2$ , assume an asynchronous ClrN as in Section 11.8. Assume  $Q_1 = Q_2 = 0$  at the beginning.

