
REQUIREMENTS NOT MET

<insert any requirements not met, i.e., problems not solved, if applicable (if not applicable, write “N/A”)>

PROBLEMS ENCOUNTERED

<insert a brief summary of *all* problems encountered>

THE ABOVE SHOULD BE LIMITED TO THE FIRST PAGE, AND
NOTHING ELSE SHOULD BE INCLUDED, WHICH ALSO IMPLIES
THAT THIS SENTENCE OF TEXT SHOULD BE REMOVED.

HOMEWORK EXERCISES

1. Complete Exercises in DAD WaveForms Tutorial

a. Exercise 1: Simple Circuit using Switches and LEDs

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

Table 1: Exercise 1 - NOR Gate Truth Table, $C = \neg(A + B)$

A(H)	B(H)	C(H)
L	L	H
L	H	L
H	L	L
H	H	L

Table 2: Exercise 1 - NOR Gate Voltage Table, $C = \neg(A + B)$

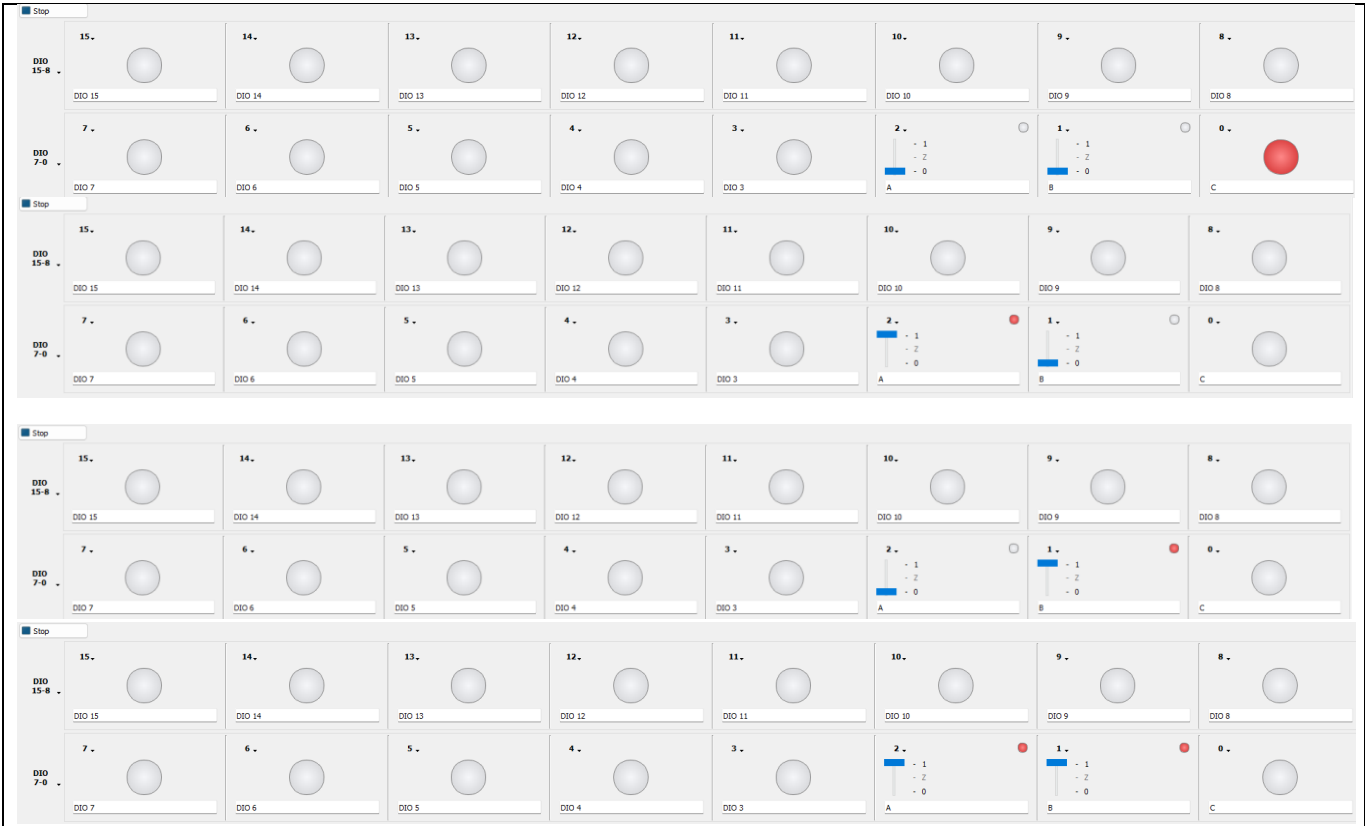


Table 3: Exercise 1 - Static I/O Results from NOR Gate

b. Exercise 2: Pattern Generator

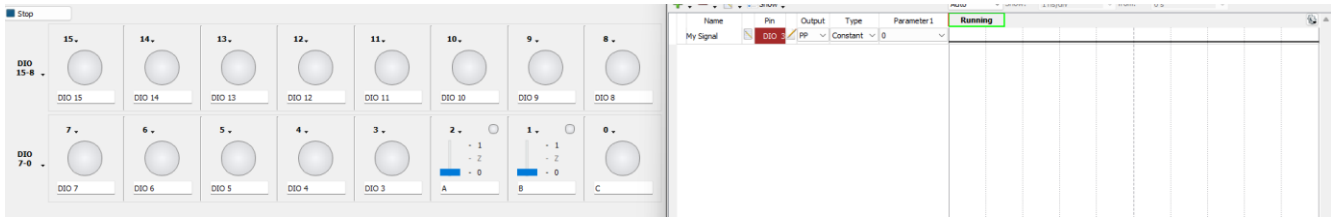


Table 4: Exercise 2 - Results from Pattern Generator Input 0

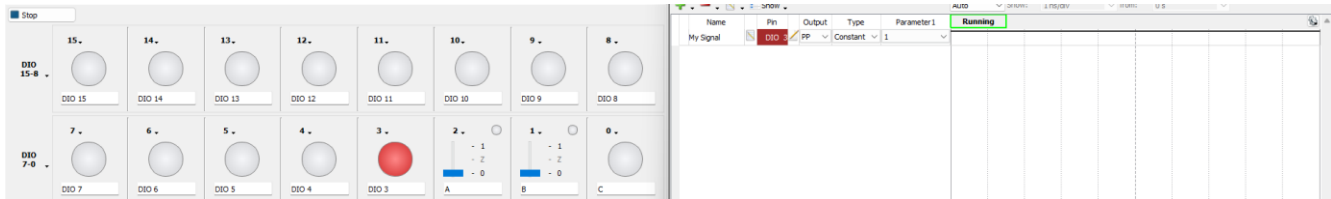


Table 5: Exercise 2 - Results from Pattern Generator Input 1

c. Exercise 3: Buses

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

Table 6: Exercise 3 - NOR Gate Truth Table, $C = \neg(A + B)$

A(H)	B(H)	C(H)
L	L	H
L	H	L
H	L	L
H	H	L

Table 7: Exercise 3 - NOR Gate Voltage Table, $C = \neg(A + B)$

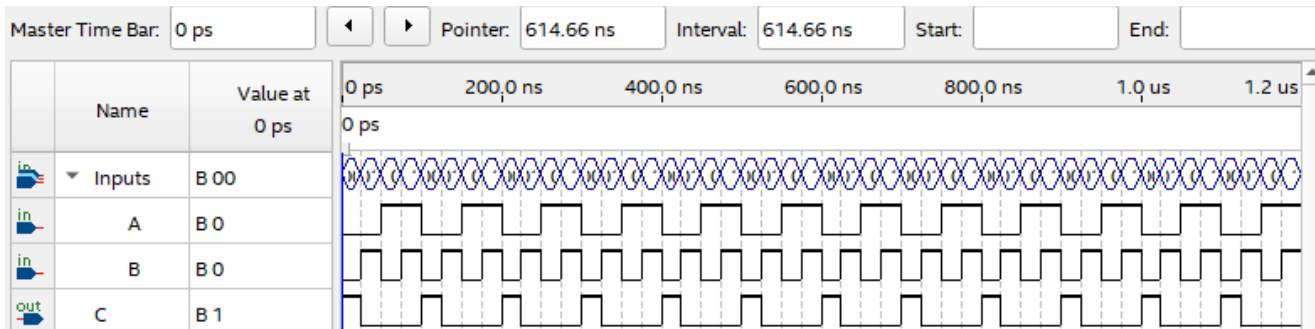


Table 8: Exercise 3 - Quartus Functional Simulation of NOR Gate

d. Logic Analyzer

 


Table 9: Logic Analyzer for Output 3

e. Setting Up a Bus

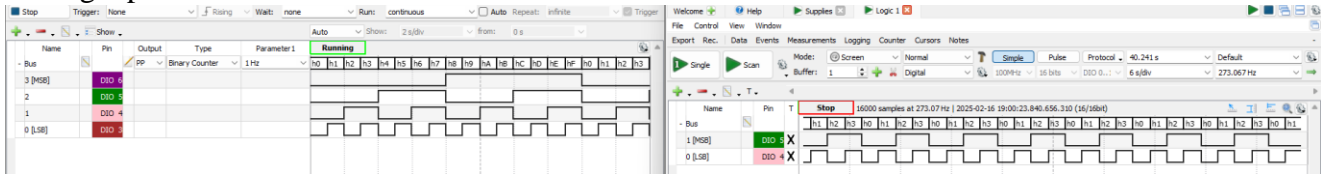


Table 10: Exercise 4 - Pattern Generator in Binary Count and Logic Analyzer with no Clock or Enable

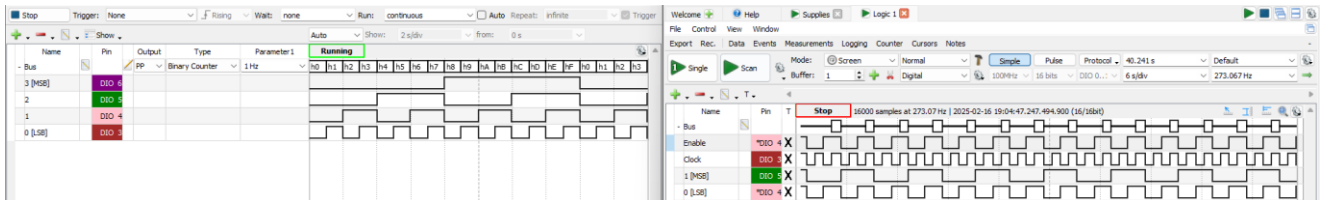


Table 11: Exercise 4 - Pattern Generator in Binary Count and Logic Analyzer with Clock DIO4 High and Enable DIO3 Rising

f. Pattern Generator Bus and Logic Analysis Bus

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

Table 12: NOR Gate Truth Table, $C = \neg(A + B)$

A(H)	B(H)	C(H)
L	L	H
L	H	L
H	L	L
H	H	L

Table 13: NOR Gate Voltage Table, $C = \neg(A + B)$

 


Table 14: Logic Analysis of NOR Gate

g. Kk;l

2. Quartus

 


Table 15: Quartus Functional Smulation of MUX

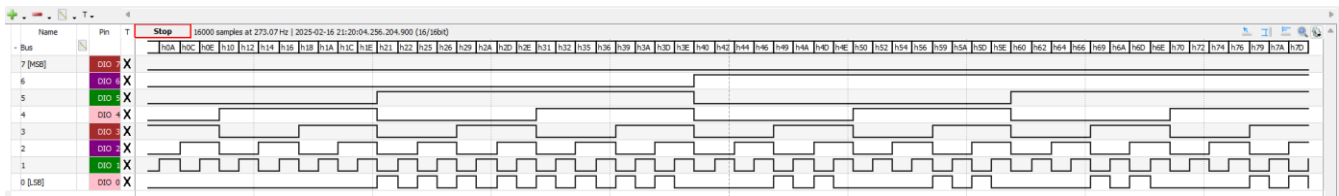


Table 16: WaveForm Logic Analysis of MUX

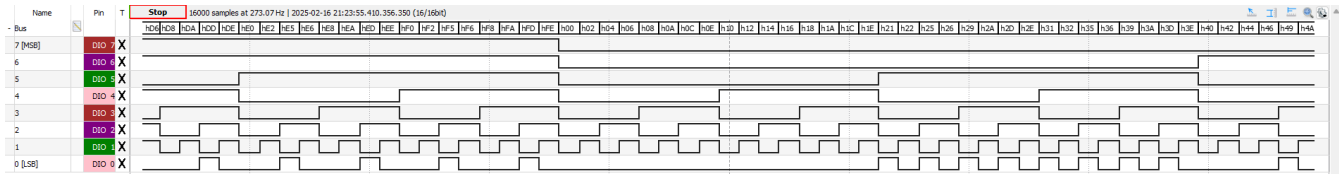


Table 17: Waveform Logic Analysis of MUX

 


Table 18: MUX Logic Analysis of MUX with specified inputs

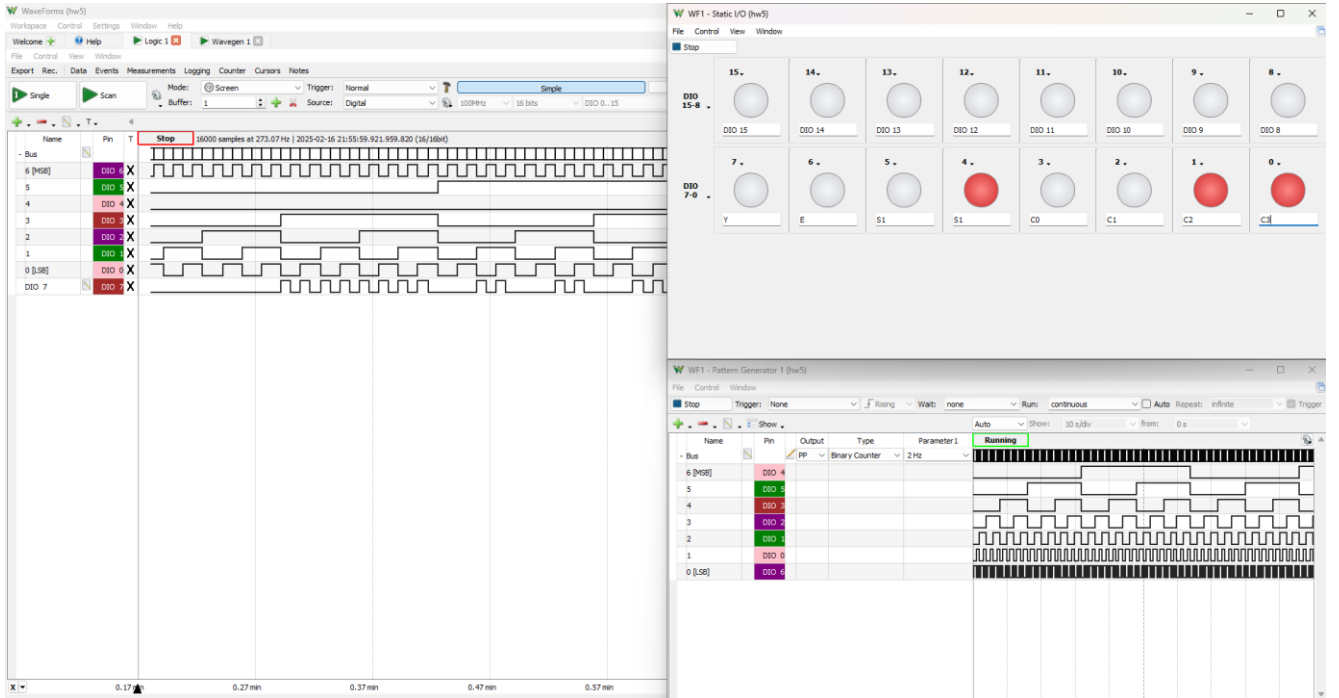


Table 19: MUX Logic Analysis of MUX with More of the Setup