

Problem

You have **60 minutes** to design a counter that counts the sequence 3, 0, 2 (repeat).

Instructions

1. Draw a next state truth table to count the sequence: 3, 0, 2 (repeat).
 - a. The counter should asynchronously start at 3 with START.
 - b. Use a JK-FF for the Msb, and D-FFs for all other bits.
2. Use K-maps to create MSOP or MPOS equations that describe the inputs to your flip-flops
3. Design and simulate your circuit in Quartus.
4. Use your debounced switch for your circuit.
5. Use your DAD for START input and for all of the outputs.

Submit to Lab - Quiz 3 - Generic

1. Screenshot of Quartus BDF.
2. Screenshot of simulation output (no need to annotate).
3. Your Quartus .qar file.

Submit to Lab - Quiz 4 - Phone

1. Scan of your breadboard and scratch paper (hand-drawn circuit, voltage table, truth table, switch and LED legends).