
REQUIREMENTS NOT MET

N/A

PROBLEMS ENCOUNTERED

When switching between devices from MAX V back to MAX X, there were some compilation errors, where I would have to select from “Device | Available Devices” in order to successfully compile when switching back from MAX V.

HOMWORK EXERCISES

- I. Creating a Project In Quartus
 - a. A New Project Design Creation
 - i. N/A
 - ii. N/A
 - iii. N/A
 - iv. N/A
 - v. N/A
 - vi. N/A
 - vii. N/A
 - viii. N/A
 - b. Configuring Quartus Window
 - i. N/A
 - ii. N/A
- II. Designing
 - a. Creating A BDF
 - i. N/A
 - ii. N/A
 - iii. N/A
 - b. Adding Text
 - i. N/A
 - ii. N/A
 - iii. N/A
 - iv. N/A
 - v. N/A
 - vi. N/A
 - vii. N/A
 - viii. N/A
 - c. Component Selection Process and Moving Components
 - i. N/A
 - ii. N/A
 - iii. N/A
 - iv. N/A
 - v. N/A
 - vi. N/A
 - vii. N/A
 - viii. N/A
 - ix. N/A
 - x. N/A
 - xi. N/a
 - xii. N/A
 - d. Adding/Deleting Wires
 - i. N/A
 - ii. N/A
 - iii. N/A

- iv. N/A
- v. N/A
- vi. N/A
- e. Adding Input and Output Ports
 - i. N/A
 - ii. N/A
 - iii. N/A
 - iv. N/A
 - v. N/A
 - vi. N/A

Homework 1 Tutorial
Name: Natalie Poche
Class: 11198
PI Name: Jaideen Magnan
Description: $Y = A * /B + /C$

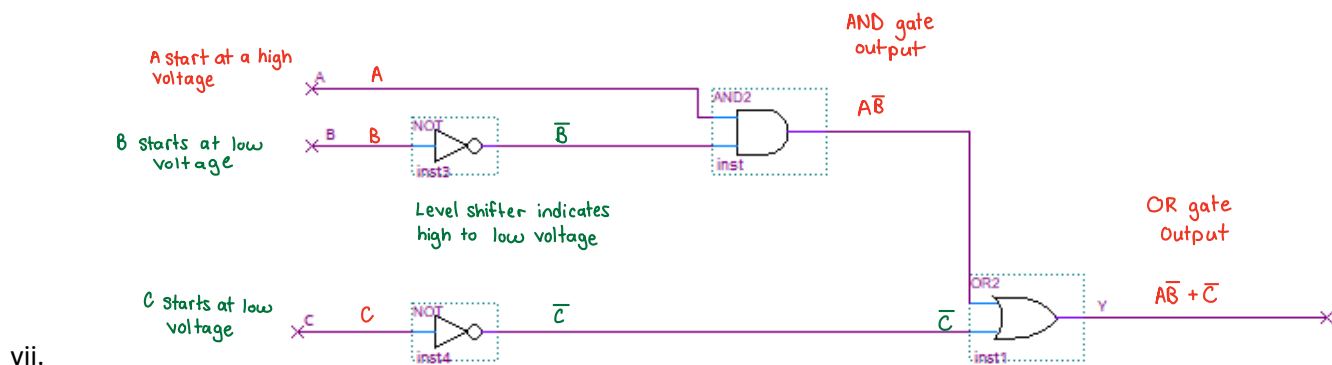
 


Figure 1: BDF with inputs and outputs

- f. Full Compilation (for programming your PLD)
 - i. N/A
 - ii. N/A
- g. Functional Compilation (for simulation only)
 - i. N/A
 - ii. N/A

III. Simulating

- a. Creating a VWF (Vector Waveform)
 - i. N/A
 - ii. N/A
- b. Adding Signals
 - i. N/A
 - ii. N/A
 - iii. N/A
- c. Changing Grid Size and End Table Time
 - i. N/A
 - ii. N/A
- d. Manually Changing VWF
 - i. N/A

- ii. N/A
- iii. N/A
- iv. N/A
- v. N/A
- e. Functional and Timing Simulation
- i. N/A

A_H	B_L	C_L	Y_H = A * /B + /C
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Figure 2: Logic Table for $Y = A * /B + /C$

A_H	B_L	C_L	Y_H = A * /B + /C
L	L	L	H
L	L	H	L
L	H	L	H
L	H	H	L
H	L	L	H
H	L	H	H
H	H	L	H
H	H	H	L

Figure 3: Voltage Table for $Y = A * /B + /C$

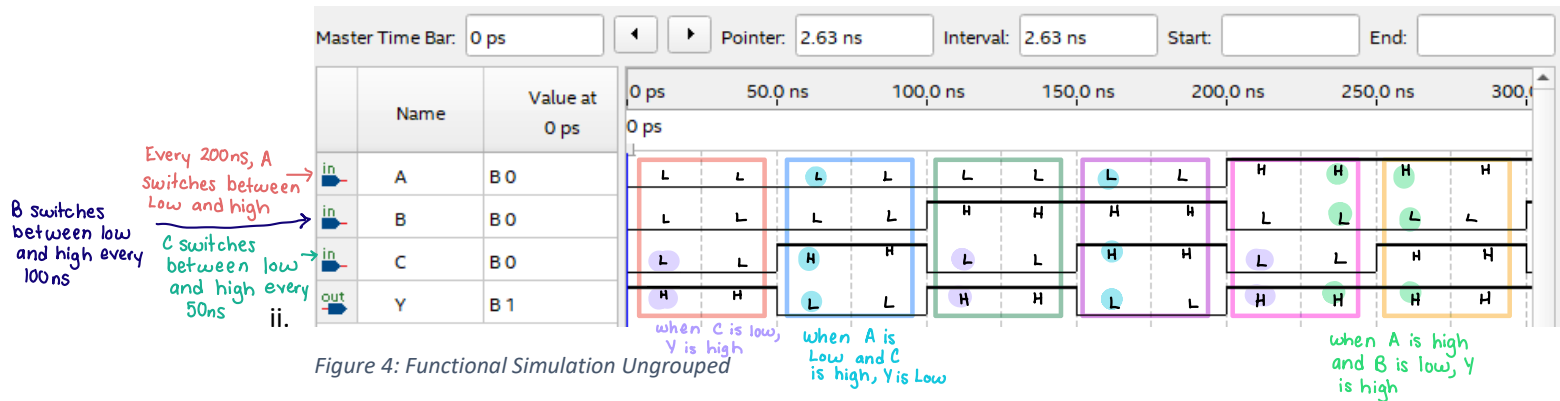


Figure 4: Functional Simulation Ungrouped

- iii. N/A
1. N/A
2. N/A
3. N/A

4. N/A
5. N/A

 


Figure 5: Time Simulation Ungrouped

Everything has the same pattern, however Y is slightly delayed, so it is off when compared to the inputs

- iv. N/A
- v. N/A
- vi. N/A
- vii. N/A
- f. Grouping Signals and Using Count Value and Clock Value
- i. N/A
- ii. N/A
- iii. N/A
- iv. N/A
- v. N/A

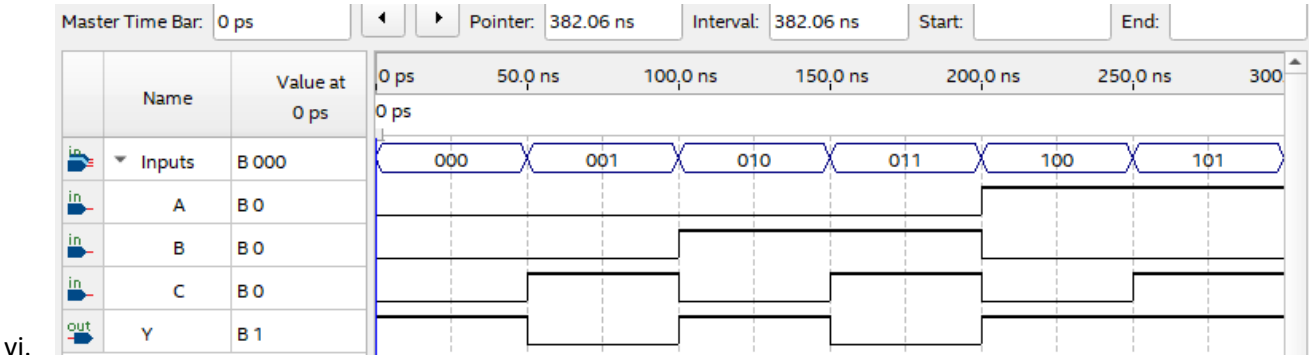


Figure 6: Functional Simulation Grouped

 


Figure 7: Time Simulation Grouped

V. Archiving Your Project

- a. Archiving your project into a qar file
 - i. N/A
 - ii. N/A
- b. Un-archiving (restoring) your project into a qar file
 - i. N/A
 - ii. N/A
 - iii. N/A